



Will the bulb light in the circuits below? Put a ring around will or will not for each circuit and complete the sentence.



The bulb will / will not light because...



The bulb will / will not light because...



The bulb will / will not light because...



The bulb will / will not light because...

Draw a circuit diagram to show one way of lighting two bulbs with one battery.